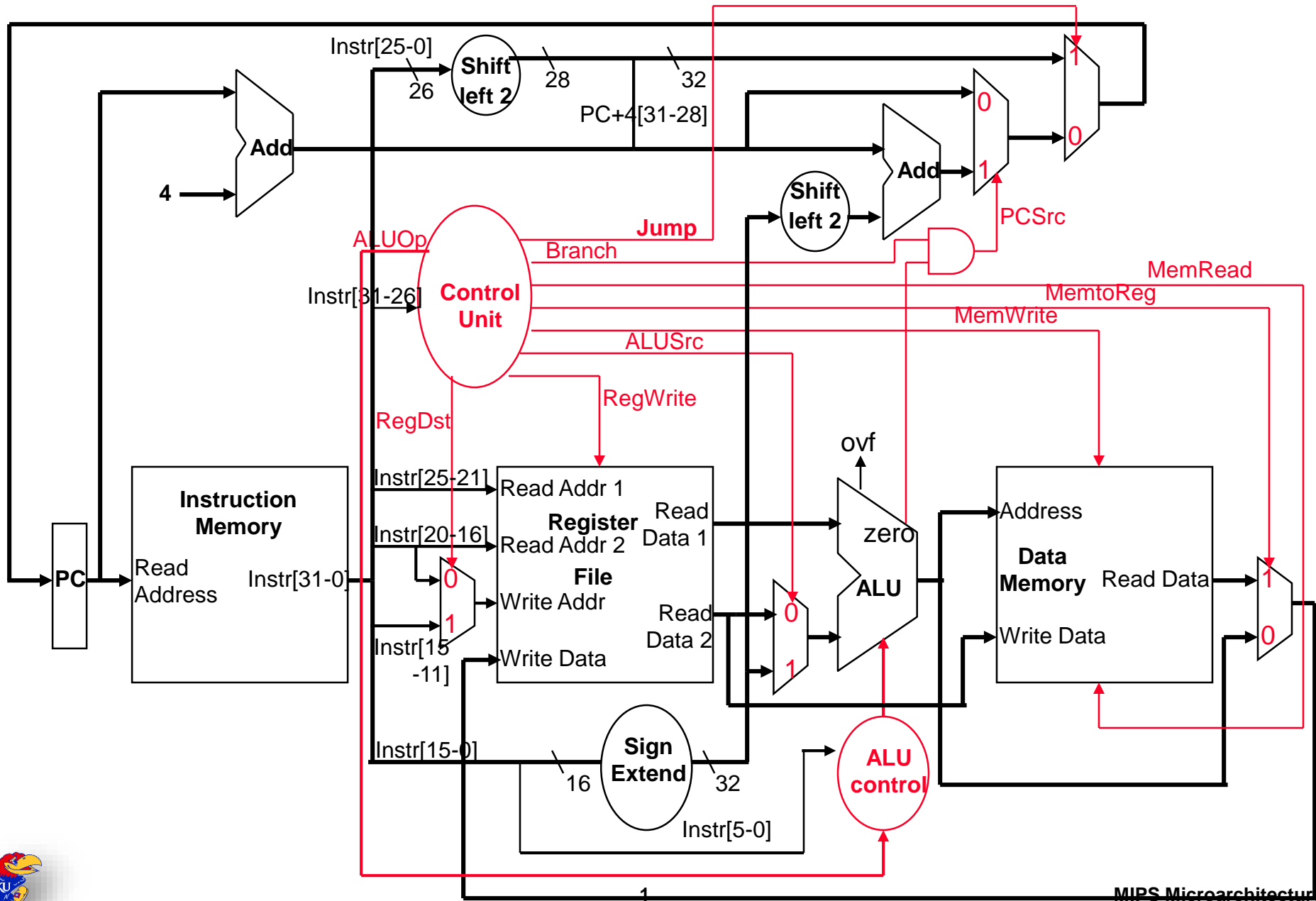


# Complete Single-Cycle Datapath



# Main Control Unit

Instr. OP	RegDst	ALUSrc	MemToReg	RegWr	MemRd	MemWr	Branch	ALUOp	Jump
<b>R-type</b> 000000	1	0	0	1	0	0	0	10	0
<b>lw</b> 100011	0	1	1	1	1	0	0	00	0
<b>sw</b> 101011	X	1	X	0	0	1	0	00	0
<b>beq</b> 000100	X	0	X	0	0	0	1	01	0
<b>j</b> 000010	X	X	X	0	0	0	X	XX	1
<b>addi</b> 001000	0	1	0	1	0	0	0	00	0

- Setting of the MemRd signal (for R-type, sw, beq, j) depends on the memory design (could have to be 0 or could be a X (don't care))



# Control Unit Logic

□ From the truth table can design the Main Control logic

